



AKSHEYAA COLLEGE OF ENGINEERING

Puludivakkam, (Near Nelvay Junction), Maduranthagam Taluk,
Kancheepuram 603 314, Tamil Nadu, India.
Phone: + 91 44 27568004-02-05, email: principal@ace.ac.in
(An ISO 9001:2008 Certified Institution)



DEPARTMENT OF SCIENCE & HUMANITIES

Branch: CSE

I Year / II Semester

Subject Code / Name: CS6201/ DIGITAL PRINCIPLES & SYSTEM DESIGN

UNIVERSITY QUESTIONS

PART-A

UNIT -1

BOOLEAN ALGEBRA AND LOGIC CIRUIT

- 1) Convert (0.6875) to binary. (May-15)
- 2) Prove the following using DeMorgan's theorem. $((x+y)' + (x+y)')' = x+y$. (May-15)
- 3) Find the octal equivalent of hexadecimal number ABCD. (May -14)
- 4) State and prove the consensus theorem. (May-14)
- 5) State the principle of duality. (Nov-14)
- 6) Implement AND gate using only NOR gates. (Nov-14)
- 7) Convert 231.3 to binary. (May-14)
- 8) Simplify $Z = (AB+C)(B'D+C'E') + (AB+C)'$. (May-14)
- 9) Realize $G = AB'C+DE+F'$ using NAND gates. (May-14)
- 10) Convert $(1001010.1101001)_2$ to base 16 and $(231.07)_8$ to base 10. (Nov-13)
- 11) Realize XOR gate using only 4 NAND gates. (Nov-13)
- 12) Convert $(101101.1101)_2$ to decimal and hexadecimal form. (May-13)
- 13) What are the limitations of Karnaugh Map? (May-13)
- 14) Find the complement and dual of $F = (y'z' + yz)$. (Nov-12)
- 15) Realize OR gate using only NAND gates. (Nov-12,05)
- 16) Write the applications of Gray code? (May-12)
- 17) Perform the following code conversion. $(1010.10)_2 = (?)_{16} \rightarrow (?)_8 \rightarrow (?)_{10}$. (Nov-11)
- 18) State the different ways for representing the signed binary numbers. (Nov-11)
- 19) Simplify the expression $((AB'+ABC)' + A(B+AB'))'$. (Nov-11)
- 20) Write the truth table of logical AND and XOR gates. (May-11)
- 21) Represent the decimal numbers -200 and 200 using 2's complement binary form. (May-11)
- 22) State and prove Consensus theorem. (Nov-10)
- 23) Find the octal equivalent of hexadecimal number. $(AB.CD)_H$. (Nov-10)
- 24) Simplify the following Boolean functions to a minimum number of literals.
(a) $(x+y)(x+y')$ (b) $xy+x'z+xz$ (May-10,07, Nov-08)
- 25) Convert the $(153.513)_{10}$ to octal. (May-10)

- 26) State the duality principle. (May-10)
- 27) Draw the logic diagram for the Boolean expression $((A+B)C)'D$ using NAND gates. (Nov-09)
- 28) Simplify the following Boolean function by K-map. $F(A,B,C,D) = \sum m(1,5,9,12,13,15)$. (May-15)
- 29) Simplify the following Boolean expression to a minimum number of literals. $AB+ACD+ABD+ABCD$. (May-09)
- 30) Show that $A+A'B=A+B$ using the theorems of Boolean Algebra. (Nov-05)
- 31) Convert $(126)_{10}$ to octal number & Binary number. (Nov-15)
- 32) Write short notes on Weighted Binary codes. (Nov-15)

UNIT – II
COMBINATIONAL LOGIC

- 33) Discuss NOR operation with a truth table. (Nov-15)
- 34) Draw the truth table of Half adder. (Nov-15)
- 35) Implement a full adder with 4×1 Multiplexer. (May-15)
- 36) Write the Data flow description of a 4-bit comparator. (May-15)
- 37) Implement the following Boolean function using 4:1 MUX $F(A,B,C) = \sum m(1,3,5,6)$. (Nov-14)
- 38) Implement the function $G = \sum m(0,3)$ using a 2×4 decoder. (May-14)
- 39) Draw the circuit of 2 to 1 line multiplexer. (May-14)
- 40) Realize 4-bit binary to gray code converter using EX-OR gates. (May-14)
- 41) State the difference between demultiplexer and decoder. (May-14)
- 42) Obtain the truth table for BCD to Excess-3 converter. (Nov-13)
- 43) Draw the truth table and circuit diagram of 4 to 2 Encoder. (Nov-13)
- 44) Write down the truth table of a full subtractor. (May-13)
- 45) Distinguish between a decoder and a Multiplexer. (May-13)
- 46) Implement a 4-bit even parity checker. (Nov-12)
- 47) Construct a 4×16 decoder using 3×8 decoders. (Nov-12)
- 48) With block diagram, show how a full adder can be designed by using two half adders and one OR gate. (Nov-11)
- 49) Implement a full adder with two half adders. (Nov-12)
- 50) List the modeling techniques available in HDL. (Nov-11, May-07)
- 51) Define decoder. Draw the block diagram and truth table for 2 to 4 decoder. (Nov-11)
- 52) Define logic synthesis and simulation. (May-12)
- 53) Draw the schematic of half adder logic. (May-11)
- 54) Determine the number and size of multiplexers required to implement a full adder. (May-11)
- 55) Compare the serial and parallel adder. (Nov-10)
- 56) Define Look ahead carry adder. (Nov-10)
- 57) Define priority encoder. (Nov-10)
- 58) Write a dataflow description of a 2 to 1 MUX. (Nov-10)
- 59) Obtain the Boolean functions for the output of the half subtractor. (May-10)
- 60) Write the Boolean function for 3-bit even parity generator and draw the circuit. (May-10)
- 61) What is an encoder? List its applications. (May-10)

- 62) Compare a decoder with a demultiplexer. (May-10)
 63) Draw the logic diagram for half adder. (Nov-09)
 64) What is the difference between decoder and demultiplexer. (Nov-09)
 65) Write down the difference between sequential and combinational circuit. (Nov-09, May-10)
 66) Give some applications of multiplexers. (May-09)
 67) What is the need for code conversion? Give two commonly used codes. (May-09)

UNIT – III
SYNCHRONOUS SEQUENTIAL LOGIC

- 68) Draw the diagram of T flip flop and discuss its working. (Nov-15)
 69) What is a shift register? (Nov-15)
 70) Give the block diagram of Master –Slave D flip flop. (May-15)
 71) What is a Ring counter? (May-15)
 72) Distinguish Mealy and Moore circuit. (Nov-14,10)
 73) With reference to a JK flip flop, what is racing? (Nov-14)
 74) Write the characteristics table and equation of JK flip flop. (May-14)
 75) Write any two applications of shift register. (May-14, Nov-10)
 76) Write the HDL code to realize a D flip flop. (May-14)
 77) Realize a JKFF using DFF and gates. (Nov-13)
 78) Write HDL code for up-down counter using behavioral model. (Nov-13)
 79) Derive the characteristics equation of a JKFF. (May-13)
 80) What is a Mealy circuit? (May-13)
 81) List any two mechanisms to achieve edge triggering of flip flops. (Nov-12)
 82) What is a ring counter? (Nov-12)
 83) How many flip flops are required for designing synchronous MOD 60 counter? (Nov-11)
 84) Write down the characteristics equation for JK and T flip flops. (Nov-11)
 85) Write the state transition table of JKFF. (May-11)
 86) Express the next state characteristics of D and SR flip flops. (May-11)
 87) What is the idea behind master slave JKFF? (May-10)

UNIT – IV
ASYNCHRONOUS SEQUENTIAL CIRCUIT

- 88) What is race condition? (Nov-15, May-14, Nov-11,09)
 89) Compare synchronous and asynchronous sequential circuit. (May-15)
 90) What is a critical race condition? Give example. (May-15, Nov-10)
 91) Define Hazard. (Nov-14, Nov-11)
 92) How many states are there in a 3-bit ring counter? What are they? (Nov-14)
 93) What are the types of hazards? (May-14, Nov-11,Nov-10)
 94) State the rules for state assignment. (May-14)

- 95) What are cycles and races? (May-14)
96) Define primitive flow table. (Nov-13, May-13)
97) What are static '1' hazard and static '0' hazard? (May-13)
98) Draw the block diagram of an asynchronous sequential circuit. (Nov-12)
99) Define static and dynamic hazards. (May-11)
100) Is it essential to have race free assignment? Justify. (May-10)
101) Does race condition exist in synchronous or asynchronous sequential circuit? Why? (May-10)
102) What are the steps for design of asynchronous sequential circuit? (Nov-09)

UNIT – V

MEMORY AND PROGRAMMABLE LOGIC

- 103) What is a memory address register? (Nov-15)
104) Write short notes on PLA. (Nov-15)
105) Differentiate between EEPROM and PROM. (May-15)
106) How to detect double error and correct single error? (May-15)
107) Whether PAL is same as PLA? Explain. (Nov-14)
108) What is a volatile memory? Give example. (Nov-14)
109) What is memory decoding? (May-14)
110) Define ASIC. (May-14)
111) State the difference between PAL and PLA. (May-14, Nov-11)
112) Distinguish EEPROM and flash memory. (Nov-13)
113) Compare SRAM and DRAM. (May-13)
114) Determine the number of address lines required for 512 bytes of memory and for a 2KB memory. (May-11)
115) What is programmable logic array? How does it differ from ROM? (Nov-09)

PART-B**UNIT -1****BOOLEAN ALGEBRA AND LOGIC CIRUIT****NOV/DEC 2015**

- 1) Simplify the following switching functions using Karnaugh map method and realize expression using gates $F(A,B,C,D) = \Sigma(0, 3, 5, 7, 8, 9, 10, 12, 15)$. (16marks)
- 2) Simplify the following switching functions using Quine McCluskey's tabulation method and realize expression using gates $F(A,B,C,D) = \Sigma(0, 5, 7, 8, 9, 10, 11, 14, 15)$. (16marks)

APRIL/MAY 2015

- 1) Simplify the following Boolean expression in (i) sum of product (ii) product of sum using K-map.
 $F = AC' + B'D + A'CD + ABCD$. (16marks)
- 2) Express the following function in sum of minterms and product of maxterms $F(x,y,z) = x + yz$. (8marks)

NOV/DEC 2014

- 1) Simplify the following $F(w,x,y,z) = \Sigma m(2, 3, 12, 13, 14, 15)$, using tabulation method. Implement the simplified function using gates. (16marks)
- 2) Simplify the Boolean function in sum of products (SOP) and product of sums (POS).
 $F(A,B,C,D) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$. (10marks)
- 3) Plot the following Boolean function in K-map and simplify it.
 $F(w,x,y,z) = \Sigma m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$. (6marks)

APRIL/MAY 2014

- 1) Simplify the following functions using k-map techniques. (i) $G = \pi M(0, 1, 3, 7, 9, 11)$
(ii) $f(w,x,y,z) = \Sigma m(0, 7, 8, 9, 10, 12) + \Sigma d(2, 5, 13)$. (16marks)
- 2) Minimize the expression using Quine McCluskey (Tabulation) method.
 $F = \Sigma m(0, 1, 9, 15, 24, 29, 30) + \Sigma d(8, 11, 31)$. (16marks)
- 3) Add, Subtract and Multiply the following numbers in binary 110010 and 11101. (6marks)
- 4) Minimize the following function using K-map. $F(A,B,C,D) = \Sigma m(0, 1, 2, 3, 4, 5, 6, 11, 12, 13)$. (10marks)
- 5) State and prove De Morgan's theorem for 2 variables. (6 marks)
- 6) Simplify the following function using Quine- McCluskey method.
 $f(a,b,c,d) = \Sigma m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$. (10marks)

NOV/DEC 2013

- 1) Simplify the following Boolean function using Quine-McCluskey method.
 $F(A,B,C,D,E) = \Sigma m(0, 1, 3, 7, 13, 14, 21, 26, 8) + \Sigma d(2, 5, 9, 11, 17, 24)$. (16 marks)
- 2) Simplify the given Boolean function in POS form using k-map and draw the logic diagram using only NOR gates. $F(A,B,C,D) = \Sigma m(0, 1, 4, 7, 8, 10, 12, 15) + \Sigma d(2, 6, 11, 14)$. (10marks)
- 3) Convert 78.5_{10} into binary. (3marks)

- 4) Find the dual and complement of the following Boolean expression, $xyz' + x'yz + z(xy + w)$. (3marks)

APRIL/MAY 2013

- 1) Reduce the following using Karnaugh map technique: (i) $f(A,B,C) = \sum m(0, 1, 3, 7) + \sum d(2, 5)$
 (ii) $F(w,x,y,z) = \sum m(0, 7, 8, 9, 10, 12) + \sum d(2, 5, 13)$. (16marks)
- 2) Simplify the following Boolean function using Quine-McCluskey method:
 $F(A,B,C,D,E,F) = \sum m(0, 5, 7, 8, 9, 12, 13, 23, 24, 25, 28, 29, 37, 40, 42, 44, 46, 55, 56, 57, 60, 61)$. (16marks)

NOV/DEC 2012

- 1) Simplify $F(A,B,C,D) = \sum (0, 1, 2, 5, 8, 9, 10)$ in sum of products and product of sums using k-map. (12marks)
- 2) Write notes on negative and positive logic. (4marks)
- 3) Simplify the expression $F(A,B,C,D) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$ using Quine-McCluskey method. (12marks)
- 4) Check if NOR operator is associative. (4marks)

NOV/DEC 2011

- 1) Simplify the following Boolean function F using K-map method:
- (i) $F(A,B,C,D) = \sum (1, 4, 5, 6, 12, 14, 15)$ (4marks)
- (ii) $F(A,B,C,D) = \sum (0, 1, 2, 4, 5, 7, 11, 15)$ (4marks)
- (iii) $F(A,B,C,D) = \sum (2, 3, 10, 11, 12, 13, 14, 15)$ (4marks)
- (iv) $F(A,B,C,D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$ (4marks)
- 2) Simplify the following Boolean expression to a minimum number of literals:
- (i) $\overline{AC} + ABC + A\overline{C}$ (2 marks)
- (ii) $XYZ + \overline{X}Y + XY\overline{Z}$ (2 marks)
- (iii) $XY + YZ + X\overline{Y}Z$ (2 marks)
- (iv) $A\overline{B} + ABD + \overline{ABD} + \overline{ACD} + \overline{ABC}$ (5 marks)
- (v) $BD + BCD + \overline{ABCD}$ (5 marks)

APRIL/MAY 2011

- 1) CONVERT $(1947)_{10}$ into its equivalent octal and hexadecimal representations. (10 marks)
- 2) Perform $(147-89)$ using 2's complement binary arithmetic. (6 marks)
- 3) Minimize the following expression using k-map.
 $Y = A'BC'D' + A'BC'D + ABC'D' + AB'C'D + A'B'CD'$. (10 marks)
- 4) State and prove the De Morgan's theorems. (6 marks)

NOV/DEC 2010

- 1) Simplify the following 5 variable Boolean expression using McCluskey method.
 $F = \sum m(0, 1, 9, 15, 24, 29, 30) + d(8, 11, 31)$. (16 marks)
- 2) Determine the minterm sum of product form of the switching function. $F = \sum (0, 1, 4, 5, 6, 11, 14, 15, 16, 17, 20, 22, 30, 32, 33, 36, 37, 48, 49, 52, 53, 59, 63)$. (16 marks)

APRIL/MAY 2010

- 1) Simplify the following using k-map and implement it with two-level NAND gate circuit:
 $F(A,B,C,D) = AB' + ABD + ABD' + A'C'D' + A'BC'$. **(16 marks)**
- 2) Simplify the following Boolean function by means of the tabulation method:
- 3) $P(A,B,C,D,E,F) = \Sigma (6, 9, 13, 18, 19, 25, 27, 29, 41, 45, 57, 61)$ **(12 marks)**
- 4) Simplify $xy' + y'z' + x'z'$ to a minimum number of literals. **(4 marks)**

NOV/DEC 2009

- 1) Simplify the following Boolean expression using Quine McCluskey method:
 $F = \Sigma m (0, 9, 15, 24, 29, 30) + d (8, 11, 31)$. **(16 marks)**
- 2) Implement Boolean expression for EX-OR gate using NAND and NOR gates. **(8marks)**
- 3) Prove that $(AB+C+D)(C'+D)(C'+D+E)=ABC+D$. **(4marks)**
- 4) Using 2's complement perform $(42)_{10} - (68)_{10}$. **(4marks)**


UNIT – II
COMBINATIONAL LOGIC

NOV/DEC 2015

- 1) Design a Full subtractor and derive expression for difference and borrow. Realize using gates. **(16marks)**
- 2) Design a code converter that converts a 8421 to BCD code. **(16marks)**

APRIL/MAY 2015

 - 1) Implement the following Boolean function with a multiplexer: $F(w,x,y,z) = \Sigma (2, 3, 5, 6, 11, 14, 15)$. **(8marks)**
- 2) Construct a 5 to 32 line decoder using 3 to 8 line decoder and 2 to 4 line decoder. **(8marks)**
- 3) Explain the analysis procedure. Analyze the following logic diagram. **(8marks)**



- 4) With neat diagram explain the 4-bit adder with carry look ahead. **(8marks)**

NOV/DEC 2014

- 1) Design and implement a 8421 to gray code converter. Realize the converter using only NAND gates. **(16marks)**

2) Design 2-bit magnitude comparator and write a Verilog HDL code.

(16marks)

APRIL/MAY 2014

1) Design a circuit that converts 8421 BCD code to excess-3 code.

(16marks)

2) Implement the following Boolean function using 8 to 1 multiplexer

$$F(A,B,C,D) = A'BD' + ACD + B'CD + A'C'D.$$

(16marks)

3) Design a 2-bit magnitude comparator.

(6marks)

4) Design a 2-bit binary multiplier to multiply two binary numbers and produce a 4-bit result.

(10marks)

5) Design a full adder and realize it using only NOR GATES.

(8marks)

6) Design a 4-bit parallel binary adder/subtractor.

(8marks)

NOV/DEC 2013

1) Design a combinational circuit to perform BCD addition.

(16marks)

2) Design a 4-bit magnitude comparator with three outputs: $A > B$, $A = B$, $A < B$

(12marks)

3) Construct a 4-bit odd parity generator circuit using gates.

(4marks)

APRIL/MAY 2013

1) Design a full adder using two half adders.

(16marks)

2) Design a combinational circuit to convert binary to gray code.

(16marks)


3) Implement the switching function $F = \sum m(0, 1, 3, 4, 12, 14, 15)$ using an 8 input MUX.

(16marks)

NOV/DEC 2012

1) Analyse the combinational circuit shown in below figure. Determine the truth table and the Boolean expressions governing the outputs of the circuit.

(10marks)

 

2) Explain BCD adder with a neat block diagram.

(6marks)

3) Design a BCD to excess-3 code converter using logic gates.

(12marks)

4) Draw the diagram of a 4-bit adder subtractor using full adders.

(4marks)

5) Implement $F(A,B,C,D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$ using 8X1 multiplexer.

(8marks)

6) Design a 4-bit priority encoder.

(6marks)

NOV/DEC 2009

- 1) Explain the gray code to binary converter with the necessary diagram. **(10marks)**
- 2) Design a half subtractor circuit. **(6marks)**

UNIT – III
SYNCHRONOUS SEQUENTIAL LOGIC

NOV/DEC 2015


- 1) Design a sequence detector that detects a sequence of three or more consecutive 1's in a string of bits coming through an input an input line and produces an output whenever this sequence is detected. **(16marks)**
- 2) Design a three bit synchronous counter with T flip flop and draw the diagram. **(16marks)**

APRIL/MAY 2015

- 1) A sequential circuit with two D flip flops A and B, one input x and one output z is specified by the following next- state and output equations: $A(t+1) = A' + B$, $B(t+1) = B'x$, $z = A + B'$
 - (i) Draw the logic diagram of the circuit. **(4marks)**
 - (ii) Derive the state table. **(3marks)**
 - (iii) Draw the state diagram of the circuit. **(8marks)**
- 2) Explain the difference between a state table, characteristic table and an excitation table. **(6marks)**
- 3) Consider the Design of a 4-bit BCD counter that counts in the following way: 0000,0001,0010,0011,.....,1001 and back to 0000.
 - (i) Draw the state diagram. **(4marks)**
 - (ii) List the next state table. **(4marks)**
 - (iii) Draw the logic diagram for the circuit. **(8marks)**

NOV/DEC 2014

 - 1) Design a MOD-10 synchronous counter using JK flip flops. Write execution table and state table. **(16marks)**
- 2) How race condition can be avoided in a flip flop? **(8marks)**
- 3) Design a synchronous counter using JKFF to count the following sequence 7,4,3,1,5,0,7... **(16marks)**
- 4) Realize the sequential circuit for the state diagram shown below. **(8marks)**



APRIL/MAY 2014

- 1) Implement T flip flop using D flip flop and JK flip flop using D flip flop. (16marks)
- 2) Design a synchronous counter which counts in the sequence 000,001,010,011,100,101,110,111,000 using DFF. (16marks)
- 3) Design a sequence detector to detect the input sequence 101 (overlapping). Use JKFF. (16marks)
- 4) Design a 3-bit synchronous up counter using JKFF. (6marks)
- 5) Design a 3-bit parallel in serial our shift register and write the HDL code to realize it. (10marks)

APRIL/MAY 2013

- 1) Using D flip flops design a synchronous counter which counts in the sequence 000,001,010,011,100,101,110,111,000. (16marks)
- 2) Design a shift register using JKFF. (16marks)


NOV/DEC 2012

- 1) Design a 3-bit binary counter. (10marks)
- 2) Write the HDL description of TFF and JKFF from DFF and gates. (6marks)
- 3) Design a sequential circuit suing RS flip flop for the state table given below using minimum number of flip flops. (16marks)

PRESENT STATE	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

NOV/DEC 2013

- 1) Design a synchronous counter with the following sequence: 0, 1, 3, 7, 6, 4 and repeats. Use JKFF. (16marks)
- 2) Design the sequential circuit specified by the following state diagram using TFF. (16marks)

 **NOV/DEC 2011**

- 1) Design a MOD 16 up counter using JKFF. **(16marks)**
- 2) With suitable example explain state reduction and state assignment. **(16marks)**

APRIL/MAY 2011

- 1) Design a synchronous counter using JK flip flops to count the following sequence. "1-3-15-5-8-2-0-12-6-9". **(16marks)**
- 2) A synchronous counter with four JKFF has the following connections:
 $J_A=K_A=1$; $J_B=Q_A Q_D$, $K_A=Q_A$; $J_C=K_C=Q_A Q_B$; $J_D=Q_A Q_B Q_C$ and $K_D=Q_A$ **(16marks)**

NOV/DEC 2010

- 1) Design a clocked sequential machine using TFF for the following state diagram. Use state reduction if possible. Also use straight state assignment. **(16marks)**
- 2) Using RSFF design a parallel counter which counts in the sequence 000,111,101,110,001,010,000. **(16marks)**
- 3) Design a T flip flop from logic gates. **(16marks)**

APRIL/MAY 2010

- 1) A sequential circuit with two DFF, A and B: two inputs, x and y: and one output z, is specified by the following next state and output equations: **(12marks)**

$$A(t+1) = x'y + xA$$

$$B(t+1) = x'B + xA$$

$$Z = B$$

Draw the logic diagram of the circuit, derive the state table and derive the state diagram.

- 2) How do ripple counters differ from synchronous counter? Explain. **(4marks)**
- 3) Explain how shift registers are used in serial addition with a neat diagram. **(8marks)**
- 4) Give the HDL description of master slave JK flip flop. **(8marks)**
- 5) Design a sequential circuit using RSFF for the state table given below using minimum number of flip flops. **(10marks)**

PRESENT STATE	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1


NOV/DEC 2009

- 1) Design and implement a MOD 5 synchronous counter using JKFF. (16marks)
- 2) Explain the working of master slave JKFF. (10marks)
- 3) Draw the diagram for a 3-bit ripple counter. (6marks)

UNIT – IV
ASYNCHRONOUS SEQUENTIAL CIRCUIT

NOV/DEC 2015

 - 1) Analyze the following clocked sequential circuit and obtain the state equations and state diagram. (16marks)



- 2) Design a serial adder using a full adder and a flip flop. (16marks)

APRIL/MAY 2015

- 1) Explain the Race-free state assignment procedure. **(8marks)**
- 2) Reduce the number of states in the following state diagram. Tabulate the reduced state table and draw the reduced state diagram. **(8marks)**

PRESENT STATE	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- 3) Explain the hazards in combinational circuit and sequential circuit and also demonstrate a hazard and its removal with example. **(16marks)**

NOV/DEC 2014

- 1) An asynchronous sequential circuit is described by the following excitation and output function.
 $Y = x_1x_2 + (x_1 + x_2)y$, $Z = Y$. **(16marks)**
 - (i) Draw the logic diagram of the circuit.
 - (ii) Derive the transition table and output map.
 - (iii) Describe the behaviour of the circuit.

APRIL/MAY 2014

- 1) Explain the steps for the design of asynchronous sequential circuits. **(16marks)**
- 2) Implement the switching function $F = \sum m(1, 3, 5, 7, 8, 9, 14, 15)$ by a static hazard free two level AND- OR gate network. **(16marks)**
- 3) Explain the two types of asynchronous sequential circuits with suitable examples. **(10marks)**
- 4) What is a flow table? Explain with a suitable example. **(6marks)**
- 5) What is an hazard? How to remove hazards using hazard covers in Karnaugh map? Explain. **(10marks)**

NOV/DEC 2013

- 1) What is the objective of state assignment in asynchronous circuit? Explain race free state assignment with an example. **(8marks)**
- 2) Discuss about static, dynamic and essential hazards in asynchronous sequential circuits. **(8marks)**
- 3) Design an asynchronous sequential circuit with inputs x_1 and x_2 and one output z . initially and at any time if both the inputs are 0, output is equal to 0. When x_1 or x_2 becomes 1, z becomes 1. When second input also becomes 1, $z=0$; the output stays at 0 until circuit goes back to initial state... **(16marks)**

APRIL/MAY 2013

- 1) Explain the types of hazards in digital circuits. **(8marks)**
- 2) Implement the switching function $F = \sum m(1, 3, 5, 7, 8, 9, 14, 15)$ by a static hazard free 2 level AND-OR gate network. **(8marks)**
- 3) Explain the steps for the design of asynchronous sequential circuits. **(16marks)**

NOV/DEC 2012


- 1) Explain race-free state assignment with an example. **(16marks)**
- 2) Write detailed notes on hazards in combinational circuits and sequential circuits. **(16marks)**

NOV/DEC 2011

- 1) With suitable example explain state reduction and state assignment. **(16marks)**
- 2) Write a detailed note on race free state assignment. **(16marks)**

APRIL/MAY 2011

- 1) Determine whether the following circuit has a static hazard or not. If yes design a hazard-free logic for the same input and output relation. **(6marks)**

 **NOV/DEC 2010**

- 1) Find a static and dynamic hazard free realization for the following function using (i) NAND gates. (ii) NOR gates. $F(a,b,c,d) = \sum m(1, 5, 7, 14, 15)$. **(16marks)**

APRIL/MAY 2010

- 1) Discuss in detail different types of hazards in digital circuits. **(12marks)**
- 2) Draw the block diagram of an asynchronous sequential circuit. List the steps involved in the design of an asynchronous sequential circuit. **(6marks)**

UNIT – V
MEMORY AND PROGRAMMABLE LOGIC

APRIL/MAY 2015

- 1) Implement the following two Boolean functions with a PLA. $F_1=AB'+AC+A'BC'$, $F_2=(AC+BC)'$ (10marks)
- 2) Give the internal block diagram of 4×4 RAM. (6marks)

NOV/DEC 2014

- 1) Design a BCD to Excess-3 code converter and implement using suitable PLA. (16marks)
- 2) Discuss on the concept of working and applications of semiconductor memories. (16marks)

APRIL/MAY 2014

- 1) Implement the following functions using PLA. $A(x, y, z) = \Sigma m (1, 2, 4, 6)$, $B(x,y,z) = \Sigma m (0, 1, 6, 7)$, $C(x, y, z) = \Sigma m (2, 6)$. (16marks)
- 2) The following messages have been coded in the even parity hamming code and transmitted through a noisy channel. Decode the messages, assuming that at most a single error has occurred in each codeword. (i) 1001001 (ii) 0111001 (iii) 1110110 (iv) 0011011. (16marks)

NOV/DEC 2013

- 1) Implement the following two Boolean functions using PLA with 3 inputs, 4 product terms and 2 outputs. $F_1 = \Sigma m (3, 5, 6, 7)$, $F_2 = \Sigma m (1, 2, 3, 4)$. (16marks)
- 2) Implement the two following Boolean functions using a 8×2 PROM. $F_1 = \Sigma m (3, 5, 6, 7)$ $F_2 = \Sigma m (1, 2, 3, 4)$. (6marks)

NOV/DEC 2012

- 1) Write notes on PLA and PAL. (8marks)
- 2) Write notes on RAM, its operation and its types. (10marks)

NOV/DEC 2010

- 1) Implement the switching functions $Z_1=ABDE+ABCDE+BC+DE$, $Z_2=ACE$, $Z_3=BC+DE+CDE+BD$, $Z_4= ACE+CE$ using 5×8×4 PLA. (16marks)

APRIL/MAY 2010

- 1) Design a combinational circuit defined by the following Boolean functions using a PAL: (16marks)
 $W(A,B,C,D) = \Sigma (2, 12, 13)$, $X(A,B,C,D) = \Sigma (7, 8, 9, 10, 11, 12, 13, 14, 15)$,
 $Y(A,B,C,D) = \Sigma (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$, $Z(A,B,C,D) = \Sigma (1, 2, 8, 12, 13)$
- 2) Write notes on the different types of ROM. (6marks)

NOV/DEC 2009

- 1) Write the comparison between PROM, PLA, PAL. (8marks)
- 2) Design a BCD to Excess-3 code converter and implement using PLA. (10marks)

Prepared by,
V.Lavanya, AP/ECE